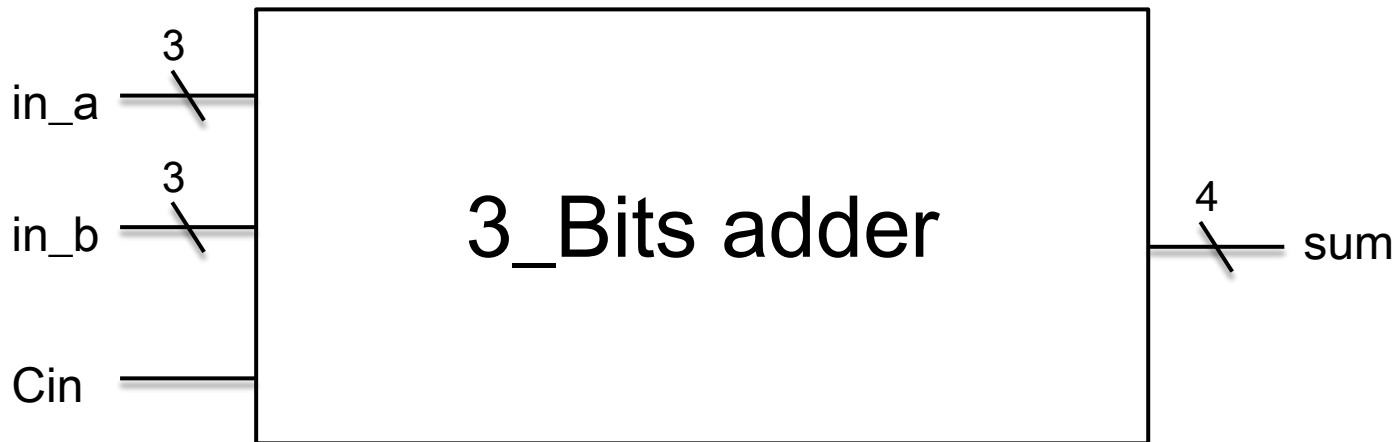




# Lab 2a : 7-Seg and Switch

1


- Design a 3\_Bits adder and demo the result on DE0 board with seven-segment display.






# Lab 2a : 7-Seg and Switch

2

 

Decimal
 
$$\begin{array}{r} 3_{10} \\ 5_{10} \\ +) 1_{10} \\ \hline 9_{10} \end{array}$$



Binary

$$\begin{array}{r} 011_2 \\ 101_2 \\ +) 001_2 \\ \hline 1001_2 \end{array}$$



# Lab 2 : 7-Seg and Switch

3

- Inputs :
  - Use 7 switches on the board to represent the value of the inputs `in_a`, `in_b` and `Cin`.
  - SW9-SW7 for `in_a`, and SW6-SW4 for `in_b`, SW0 for `Cin`.
- Outputs :
  - Show the decimal value of the inputs and outputs on seven-segment display.
  - HEX3 for `in_a`, HEX2 for `in_b`, and HEX1-HEX0 for `sum`.



# Pins-Switches

4

Signal Name	FPGA Pin No.	Description
SW[9]	PIN_D2	Slide Switch[9]
SW[8]	PIN_E4	Slide Switch[8]
SW[7]	PIN_E3	Slide Switch[7]
SW[6]	PIN_H7	Slide Switch[6]
SW[5]	PIN_J7	Slide Switch[5]
SW[4]	PIN_G5	Slide Switch[4]
SW[3]	PIN_G4	Slide Switch[3]
SW[2]	PIN_H6	Slide Switch[2]
SW[1]	PIN_H5	Slide Switch[1]
SW[0]	PIN_J6	Slide Switch[0]



# Pins-7Seg

5

Signal Name	FPGA Pin No.	Signal Name	FPGA Pin No.	Signal Name	FPGA Pin No.	Signal Name	FPGA Pin No.
HEX3_DP	PIN_G16	HEX2_DP	PIN_A18	HEX1_DP	PIN_B15	HEX0_DP	PIN_D13
HEX3_D[6]	PIN_G15	HEX2_D[6]	PIN_F14	HEX1_D[6]	PIN_A15	HEX0_D[6]	PIN_F13
HEX3_D[5]	PIN_D19	HEX2_D[5]	PIN_B17	HEX1_D[5]	PIN_E14	HEX0_D[5]	PIN_F12
HEX3_D[4]	PIN_C19	HEX2_D[4]	PIN_A17	HEX1_D[4]	PIN_B14	HEX0_D[4]	PIN_G12
HEX3_D[3]	PIN_B19	HEX2_D[3]	PIN_E15	HEX1_D[3]	PIN_A14	HEX0_D[3]	PIN_H13
HEX3_D[2]	PIN_A19	HEX2_D[2]	PIN_B16	HEX1_D[2]	PIN_C13	HEX0_D[2]	PIN_H12
HEX3_D[1]	PIN_F15	HEX2_D[1]	PIN_A16	HEX1_D[1]	PIN_B13	HEX0_D[1]	PIN_F11
HEX3_D[0]	PIN_B18	HEX2_D[0]	PIN_D15	HEX1_D[0]	PIN_A13	HEX0_D[0]	PIN_E11
HEX3		HEX2		HEX1		HEX0	