




Homework4: Sequence Detector

1

- Implement a sequence detector that can search the string “110” using Verilog HDL
- str_in (serial input) ; str_out (parallel output)

Ex: str_out : 100; match : 0
str_out : 110; match : 1

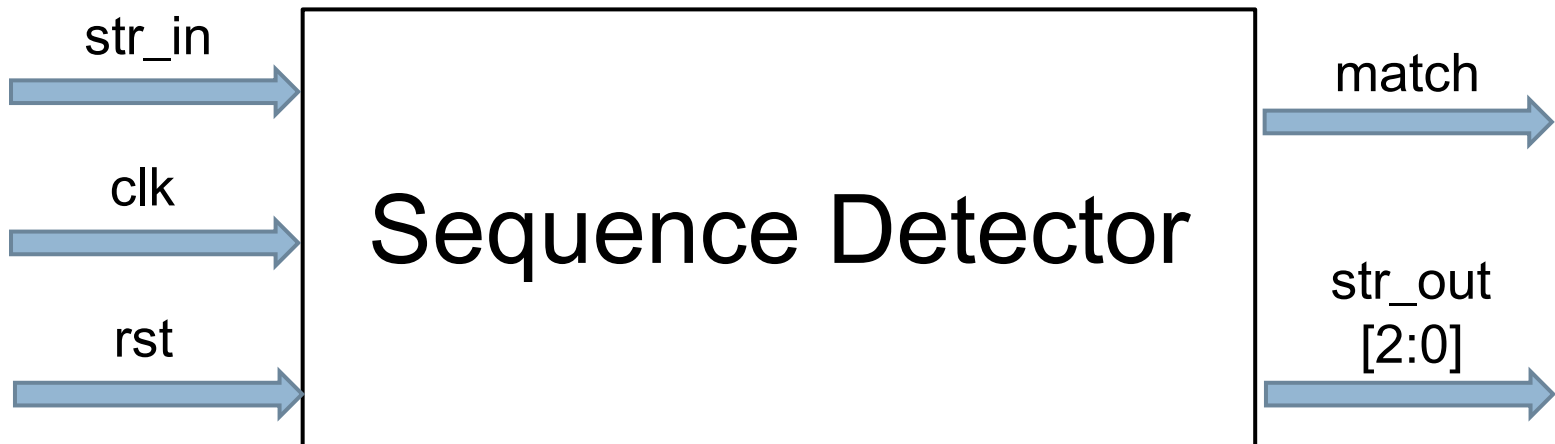




Homework4: Sequence Detector

2

□ State Transition Diagram

 



Homework4: Sequence Detector

3

```
module sequence_detector(str_out, match, rst, str_in, clk);  
    input  clk, rst, str_in, ;  
    output [2:0]str_out;  
    output match;  
  
    .....  
endmodule
```

